

Two-Stage Miller Design

Bilal Ramadan

Supervisor: Dr. Hesham Omran

Table of Contents

Part 1: OTA Design	5
1. Desired specs.....	5
2. OTA Schematic.....	6
3. OTA Devices Sizing.....	6
Part 2: Open –loop OTA simulation	7
1. OP simulation	7
2. Diff small signal ccs.....	9
3. CM small signal ccs	10
4. CMRR	11
5. Diff large signal ccs	12
6. CM large signal ccs (region vs VICM).....	13
7. CM large signal ccs (GBW vs VICM)	14
Part 3: Closed-Loop OTA Simulation	15
1. OP simulation	15
2. Loop gain	17
3. Slew rate.....	19
4. Settling time	21
Part 4: DC Closed Loop AC Open-Loop OTA Simulation.....	23
1. OP simulation	23
2. Diff small signal ccs.....	25
3. CM small signal ccs	26
4. CMRR	26
5. Diff large signal ccs	27
6. CM large signal ccs (region vs VICM).....	27
7. CM large signal ccs (GBW vs VICM)	28
Part 5: Design specs	29

Table of Figures

Figure 1:OTA schematic.....	6
Figure 2: Final design schematic.....	7
Figure 3: Open-loop testbench.....	7
Figure 4: bias circuit with DC node voltages annotated.....	8
Figure 5: OTA schematic with DC node voltages and OP parameters annotated.....	8
Figure 6: diff gain bode plot (magnitude)	9
Figure 7: diff small signal results	9
Figure 8: CM gain bode plot (magnitude)	10
Figure 9: Vout vs VID	12
Figure 10: derivative(Vout) vs VID.....	12
Figure 11: regions vs VICM	13
Figure 12: GBW vs VICM.....	14
Figure 13: Closed-loop testbench schematic (CL=5 pF, IB=10 uA)	15
Figure 14: bias circuit with DC node voltages annotated.....	15
Figure 15: OTA schematic with DC node voltages and OP parameters annotated.....	16
Figure 16: loop gain bode plot (magnitude).....	17
Figure 17: loop gain bode plot (phase).....	17
Figure 18: loop gain Gx.....	17
Figure 19: STB analysis results.....	18
Figure 20: closed loop hand analysis.....	18
Figure 21: pulse settings.....	19
Figure 22: Slew rate.....	19

Figure 23: Slew rate at $C_c=2.3$ pF	19
Figure 24: dV_{out}/dt	20
Figure 25: Transient analysis V_{in} & V_{out} vs time	20
Figure 26: pulse settings.....	21
Figure 27: rise time.....	21
Figure 28: V_{in} & V_{out} vs time.....	21
Figure 29: Testbench schematic ($C_L=5$ pF, $I_B=10$ uA).....	23
Figure 30: bias circuit with DC node voltages annotated.....	23
Figure 31: OTA schematic with DC node voltages and OP parameters annotated.....	24
Figure 32: diff gain bode plot (magnitude)	25
Figure 33: diff small signal results	25
Figure 34: CM gain bode plot (magnitude)	26
Figure 35: regions vs V_{ICM}	27
Figure 36: GBW vs V_{ICM}	28

Tables

Table 1: Desired Specs.....	5
Table 2: OTA Devices Sizing.....	6
Table 3: simulation vs hand analysis	9
Table 4: simulation vs hand analysis	10
Table 5: simulation vs hand analysis	11
Table 6: CMIR simulation vs hand analysis.....	13
Table 7: CMIR simulation vs hand analysis.....	14
Table 8: open loop vs closed loop simulation	18
Table 9: simulation vs hand analysis	20
Table 10: simulation vs hand analysis	25
Table 11: simulation vs hand analysis	26
Table 12: simulation vs hand analysis	27
Table 13: Design specs	29

Part 1: OTA Design

1. Desired specs

Technology	180 nm CMOS
Supply Voltage	1.8 V
Static gain error	$\leq 0.05 \%$
CMRR @DC	$\geq 74 \text{ dB}$
Phase Margin	$\geq 70^\circ$
OTA current consumption	$\leq 60 \mu\text{A}$
CMIR - high	$\geq 1 \text{ V}$
CMIR - low	$\leq 0.2 \text{ V}$
Output swing	0.2 V – 1.6 V
Load	5 pF
Buffer closed loop rise time (10% to 90%)	$\leq 70 \text{ ns}$
Slew rate	5 V/ μs

Table 1: Desired Specs

At first, we need to identify the topology.

Since the CMIR is near to GND, therefore the topology we will use in the Two-Stage Miller OTA is the PMOS for the 1st stage input pair and NMOS in the 2nd input stage to match VGS in order to avoid the zero systematic offset.

2. OTA Schematic

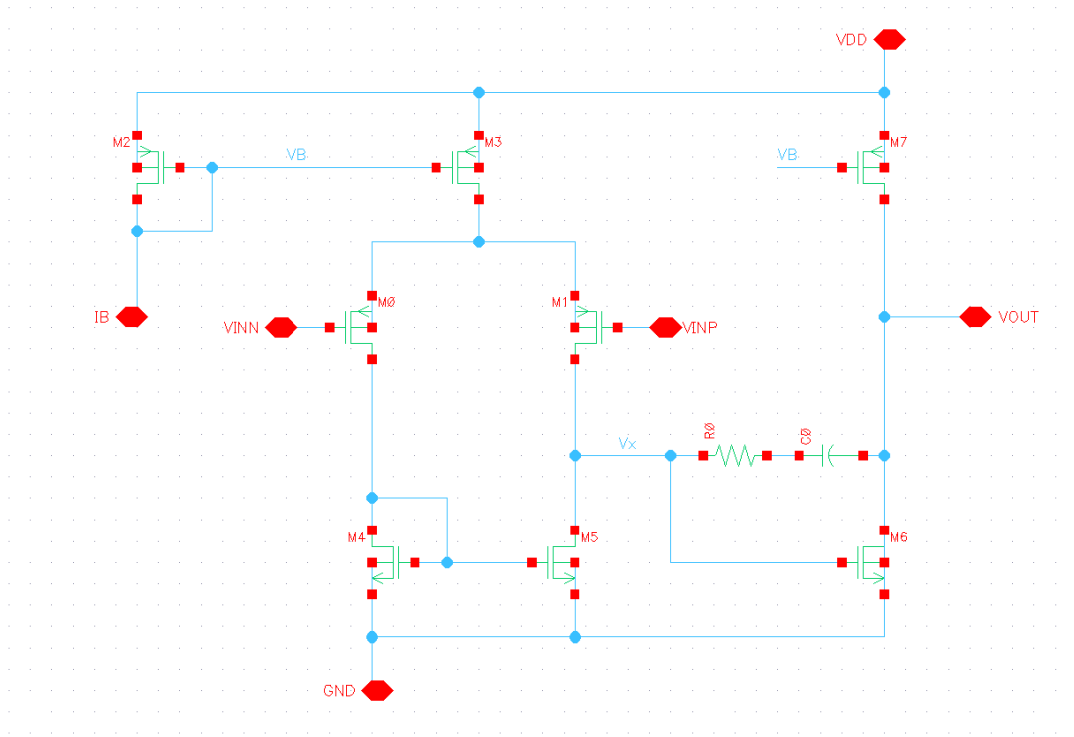


Figure 1:OTA schematic

3. OTA Devices Sizing

Device	M_2 (input CM)	M_3 (tail CM)	$M_{0,1}$ (1^{st} stage input pair)	$M_{4,5}$ (load CM)	M_6 (2^{nd} input stage)	M_7 (2^{nd} stage CM load)
W	13.24 μm	18.543 μm	26.77 μm	17.354 μm	126.38 μm	61.34 μm
L	350 nm	350 nm	720 nm	1.3 μm	1.3 μm	350 nm
g_m	140 μS	177.8 μS	95.25 μS	104.78 μS	762 μS	646.52 μS
I_D	10 μA	12.7 μA	6.35 μA	6.35 μA	46.18 μA	46.18 μA
g_m/I_D	14	14	15	16.5	16.5	14
$ V_{DSSat} $	122.4 mV	121.7 mV	105 mV	92.8 mV	92.8 mV	122.4 mV
V_{ov}	75.95 mV	75.95 mV	62.2 mV	31.6 mV	31.6 mV	75.95 mV
V^*	143 mV	143 mV	133 mV	121 mV	121 mV	143 mV

Table 2: OTA Devices Sizing

Part 2: Open –loop OTA simulation

1. OP simulation

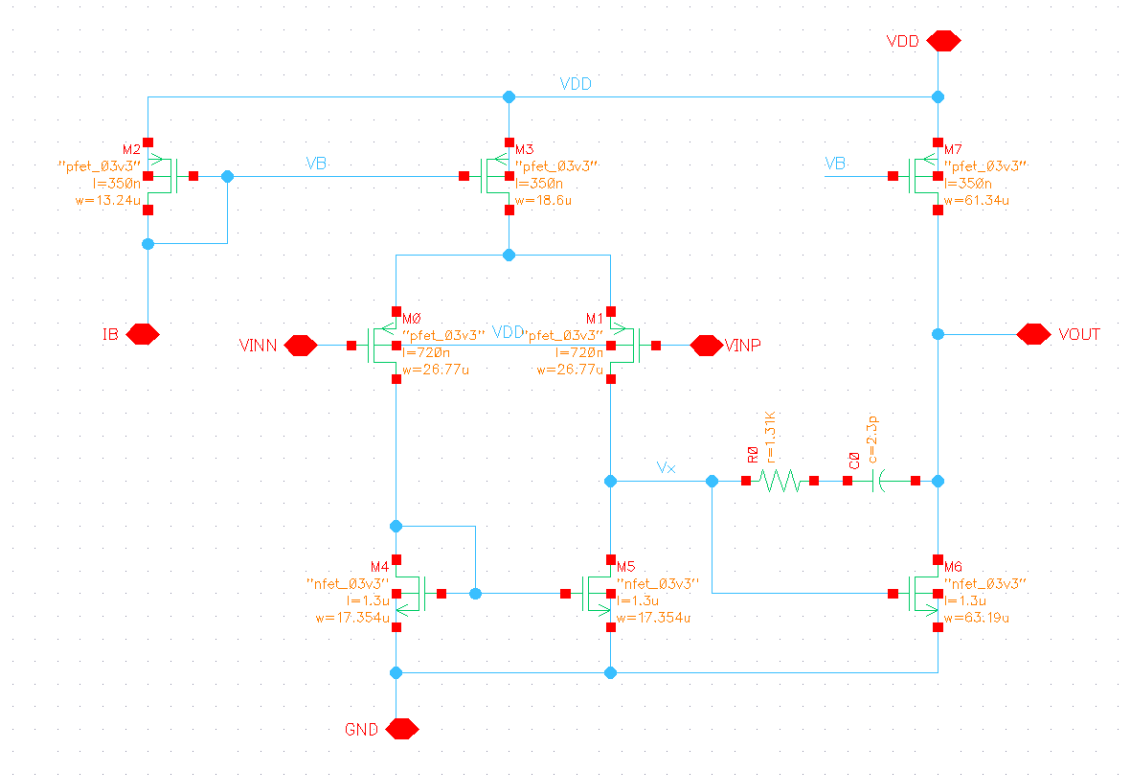


Figure 2: Final design schematic

Note: M6 has multiplier of 2.

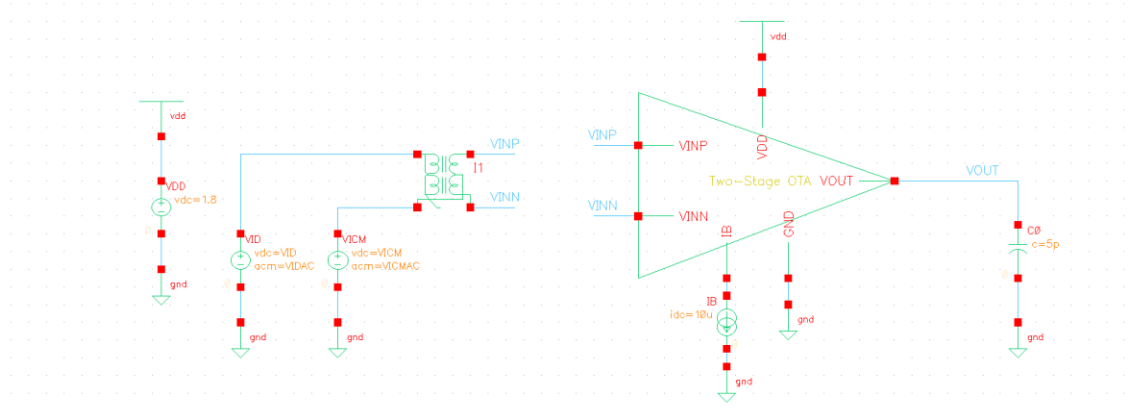


Figure 3: Open-loop testbench

- The dc level of V_{out} is 957.6 mV as it's a high impedance node so it's ill-defined but we recovered that problem by taking VDS into consideration in the ID/W charts.

2. Diff small signal ccs

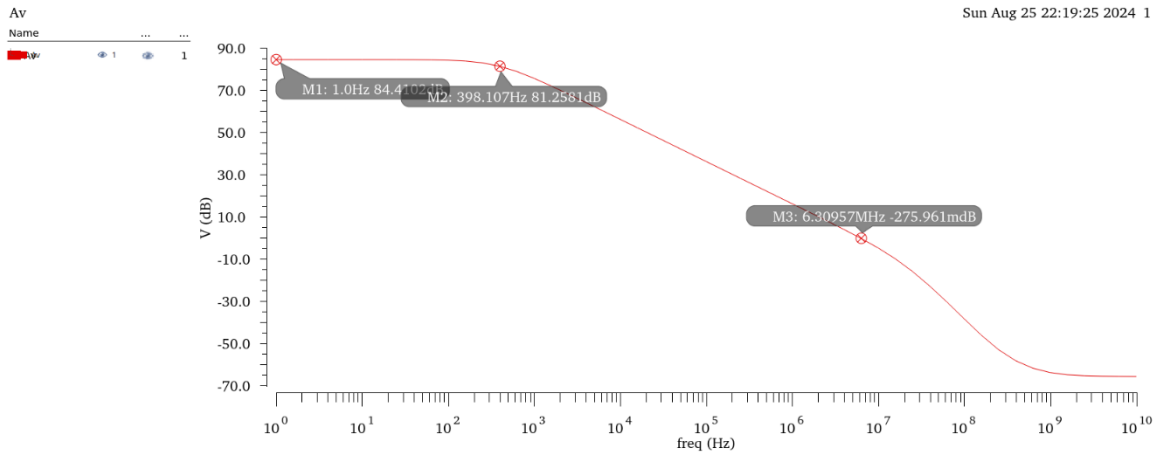


Figure 6: diff gain bode plot (magnitude)

Test	Output	Nominal	Spec
ITI_labs:lab9_TB1:1	Av	16.62k	> 2k
ITI_labs:lab9_TB1:1	Av in dB	84.41	> 66
ITI_labs:lab9_TB1:1	BW	385.4	
ITI_labs:lab9_TB1:1	Fu	6.19M	> 5M
ITI_labs:lab9_TB1:1	GBW	6.418M	

Figure 7: diff small signal results

$$DC \text{ diff gain} = g_{m0,1}(r_{o1} \parallel r_{o5}) * g_{m6}(r_{o6} \parallel r_{o7}),$$

$$BW \approx \frac{1}{2\pi(r_{o1} \parallel r_{o5}) * g_{m6}(r_{o6} \parallel r_{o7})C_c}, GBW = \frac{g_{m0,1}}{2\pi C_c}$$

Spec	Simulation	Hand analysis
DC diff gain	84.41 dB	84.42 dB
BW	385.4 Hz	391 Hz
GBW	6.4 MHz	6.6 MHz

Table 3: simulation vs hand analysis

- UGF and GBW are almost the same and that's an indicator to a good PM.
- BW & GBW hand analysis are different from the simulation as the parasitic caps are large due to the large sizes and they are not taken into consideration in the hand analysis.

- The dc diff gain is way larger than the spec as the input pair suffer from body effect so we biased them at large g_m/I_D to make their V_{GS} smaller to get near from $CMIR_{high}$ spec and larger g_m/I_D for the 2nd stage NMOS to meet the PM spec (ratios of $g_m \geq 8$) as we can't use small current in the 1st stage due to the SR spec and can't use larger current in the 2nd stage due to current consumption spec. And the load CM has high gm/gds to meet the gain we need at the 1st stage to meet the CMRR which are matched to the 2nd stage NMOS to avoid the systematic zero offset. And the three upper PMOS devices are matched as they are CMs and the one in the 1st stage has condition on g_{ds} to meet the CMRR spec so the load CM of the 2nd stage is small So the 2nd stage has higher gain than wanted.

3. CM small signal ccs

 


Figure 8: CM gain bode plot (magnitude)

Test	Output	Nominal
ITI_labs:lab9_TB1:1	Av _{cm}	1.093
ITI_labs:lab9_TB1:1	Av _{cm} in dB	776m

Figure 26: CM gain

$$DC \text{ CM gain} \approx \frac{-g_{m0,1}}{2(g_{m0,1} + g_{mb0,1})g_{m4,5}r_{o3}} * g_{m6}(r_{o6} \parallel r_{o7})$$

Spec	Simulation	Hand analysis
DC CM gain	1.093	1.11

Table 4: simulation vs hand analysis

4. CMRR

 


Figure 27: CMRR bode plot (magnitude)

Spec	Simulation	Hand analysis
CMRR @DC	83.6 dB	$A_{vd} - A_{vcm} = 83.5 \text{ dB}$

Table 5: simulation vs hand analysis

5. Diff large signal ccs

DC Analysis 'dc': VID = (-100e-03 -> 100e-03)

 


Figure 9: V_{out} vs VID

$V_{outdc} = 957.55 \text{ mV}$ almost the same from the OP part (957.6 mV) as there is no mismatch nor diff input.

dVout/dVI

Thu Aug 22 19:01:31 1

 


Figure 10: $\text{derivative}(V_{out})$ vs VID

The peak = 941.3 $\ll A_{vd}$ due to the very small swing of the differential input (equals output swing/ $A_{vd} = \frac{1.6}{16.62k}$) so the diff input swing is less than 0.1 mV and the step is 1 mV only so the results are inaccurate.

6. CM large signal ccs (region vs VICM)

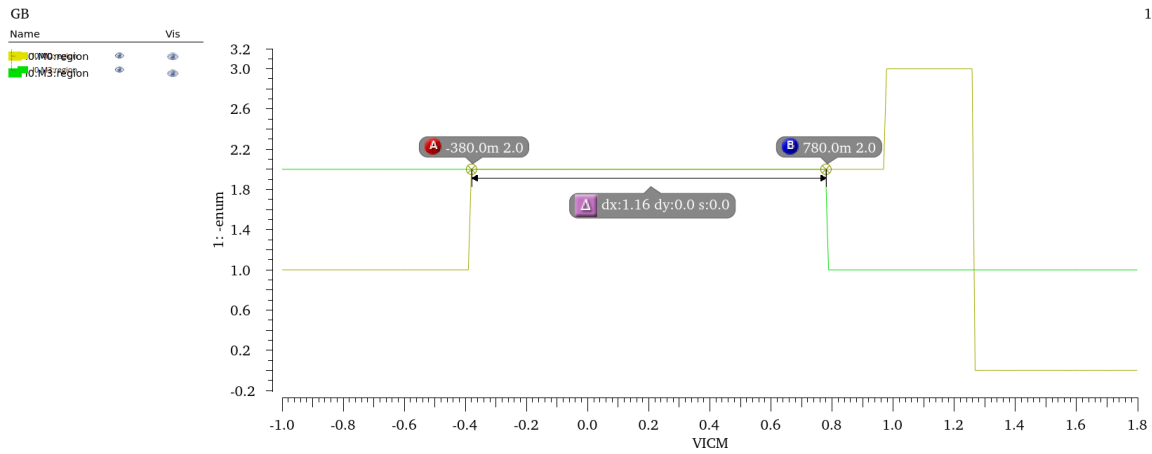


Figure 11: regions vs VICM

$$CMIR_{high} = V_{DD} - |V_{DSsat3}| - |V_{GS0,1}|$$

$$CMIR_{low} = -|V_{GS0,1}| + |V_{DSsat0,1}| + V_{GS4,5}$$

<i>Spec</i>	<i>simulation</i>	<i>analytic</i>
$CMIR_{low}$	-380 mV	-143 mV
$CMIR_{high}$	780 mV	693 mV

Table 6: CMIR simulation vs hand analysis

7. CM large signal ccs (GBW vs VICM)

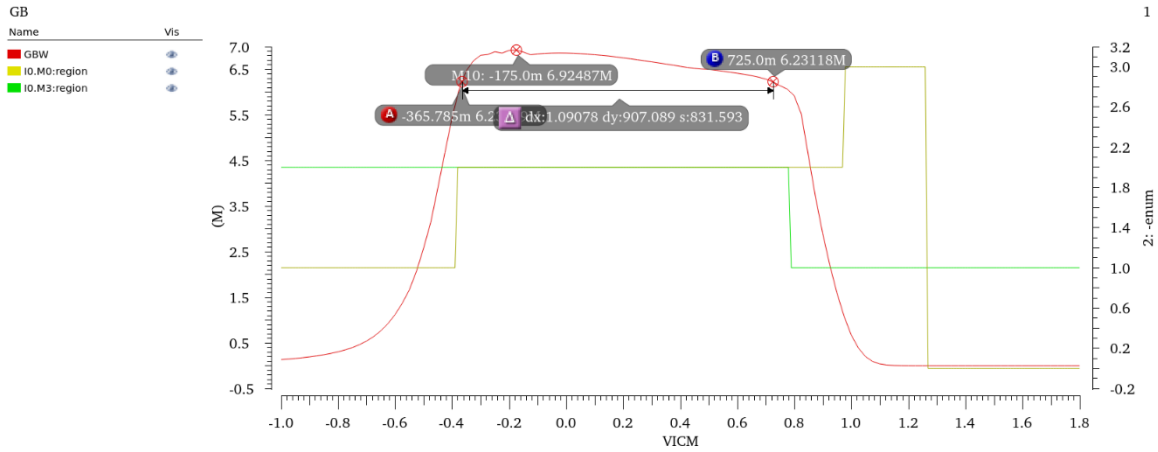


Figure 12: GBW vs VICM

$$CMIR_{high} = V_{DD} - |V_{DSsat3}| - |V_{GS0,1}|$$

$$CMIR_{low} = -|V_{GS0,1}| + |V_{DSsat0,1}| + V_{GS4,5}$$

Spec	simulation	analytic
$CMIR_{low}$	-365 mV	-143 mV
$CMIR_{high}$	725 mV	693 mV

Table 7: CMIR simulation vs hand analysis

The noticeable variance in the $CMIR$ is due to:

- The 90 % change in GBW is not an accurate value to detect the edge of saturation for the Diff Amp devices because the saturation happens gradually not eventually at a specific point.
- The body effect obstacles the $CMIR_{high}$ but it also advances $CMIR_{low}$ as the VGS increases and it appears in both specs in negative.

Part 3: Closed-Loop OTA Simulation

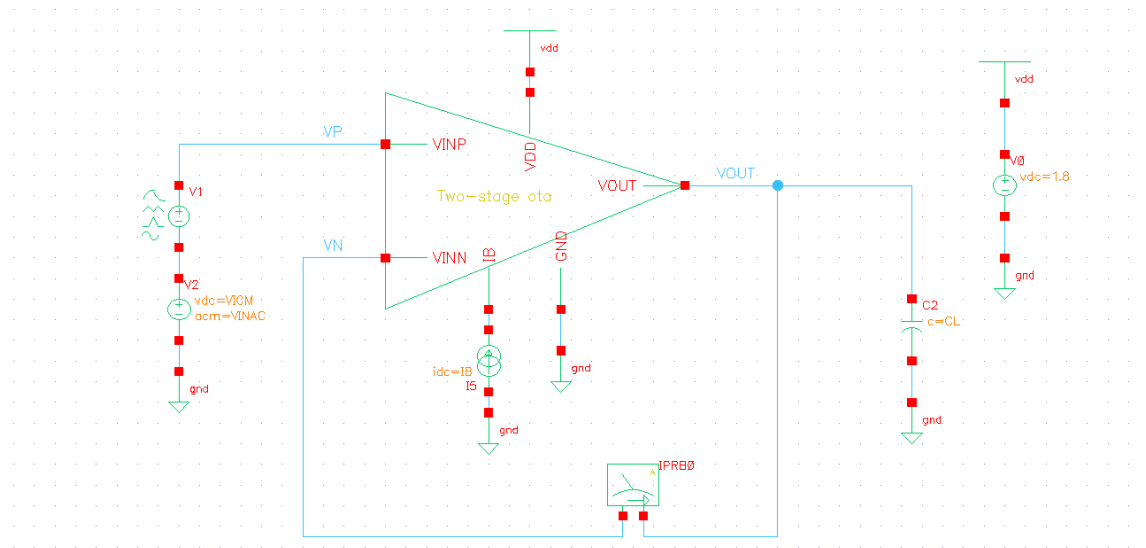


Figure 13: Closed-loop testbench schematic ($CL=5\text{ pF}$, $IB=10\text{ uA}$)

1. OP simulation

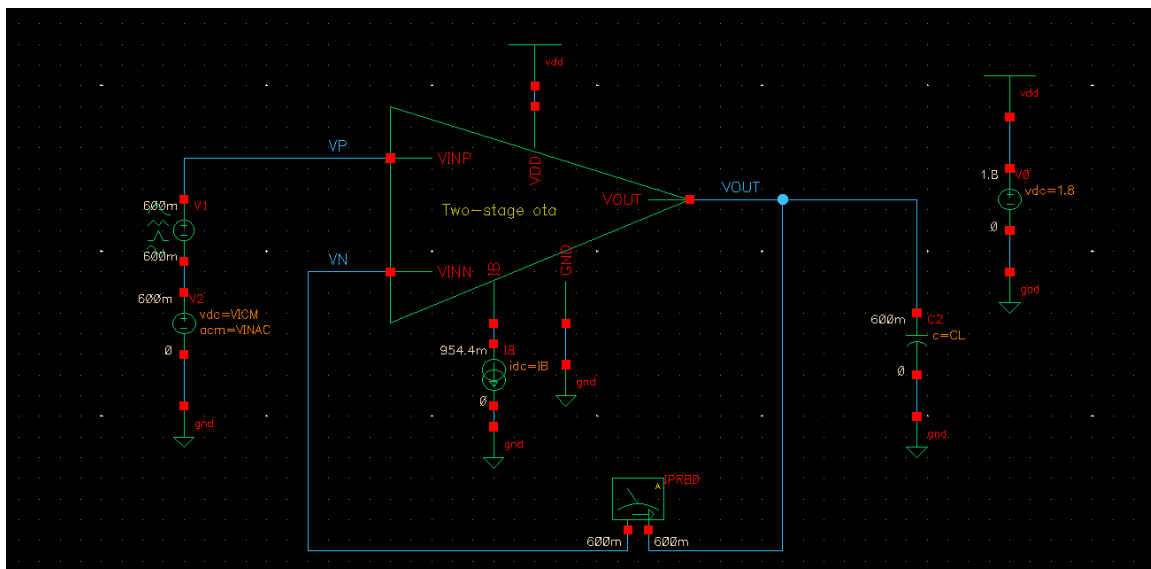


Figure 14: bias circuit with DC node voltages annotated

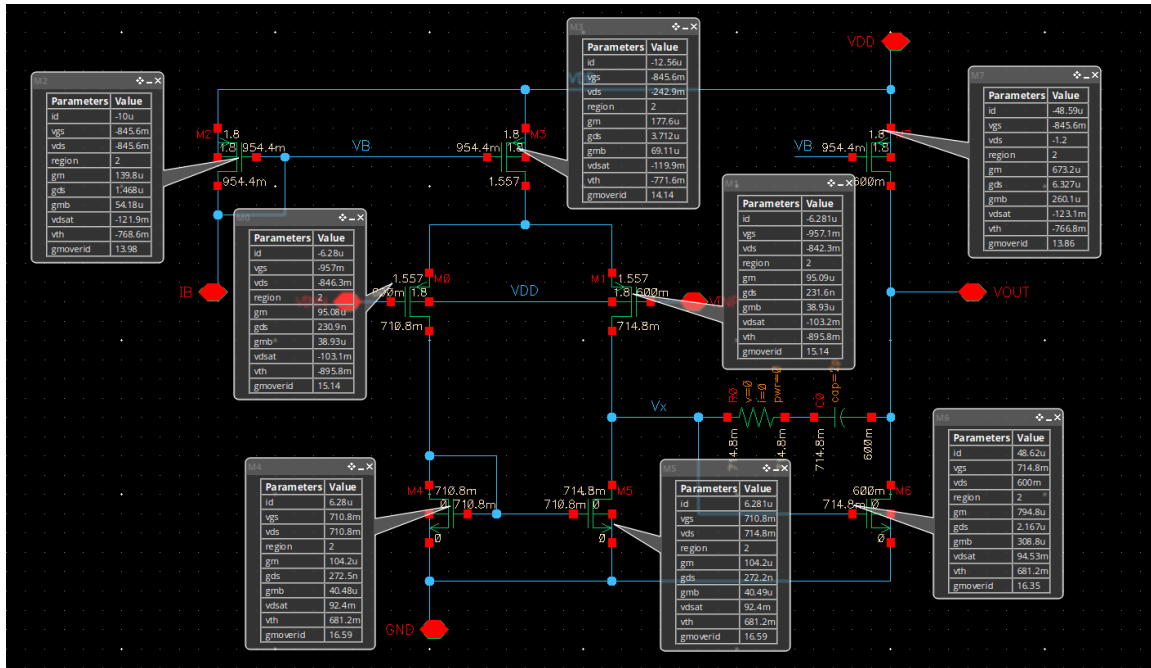


Figure 15: OTA schematic with DC node voltages and OP parameters annotated

- The voltage difference across the OTA's terminals (differential input/error signal) is nearly zero due to the very high open-loop gain which minimizes the error signal. As the error signal equals the output deviation from its dc level divided by the amplifier's open-loop gain = $\frac{(957.6-600) \text{ mV}}{16.62 \text{ K}} \approx 21.5 \text{ } \mu\text{V}$.
- The output of the 1st stage dc level is different from its value in the open-loop simulation as the gain of the 2nd stage alone is finite and the error at this node is the output deviation from its dc level divided by the 2nd stage gain $\frac{(957.6-600) \text{ mV}}{93} \approx 3.8 \text{ mV}$.
- The change in g_m and I_D (about 0.02%) is due to the amplifier's very high open-loop gain which minimizes the error across its input terminals.

2. Loop gain

 


Figure 16: loop gain bode plot (magnitude)

 


Figure 17: loop gain bode plot (phase)

 


Figure 18: loop gain Gx

Test	Output	Nominal	Spec
ITI_labs:lab9_TB2:1	dc loop gain	17.64k	> 2k
ITI_labs:lab9_TB2:1	dc loop gain in dB	84.93	> 66
ITI_labs:lab9_TB2:1	BW	363.1	
ITI_labs:lab9_TB2:1	Fu	6.167M	> 5M
ITI_labs:lab9_TB2:1	GBW	6.42M	> 5M
ITI_labs:lab9_TB2:1	PM	70.33	> 70

Figure 19: STB analysis results

The open-loop results changed as Cc value changed as said in the report in the few coming pages.

Spec	open loop simulation	closed loop simulation
DC gain	84.41 dB	84.93 dB
BW	385.4 Hz	363.1 Hz
GBW	6.4 MHz	6.4 MHz

Table 8: open loop vs closed loop simulation

The specs variance between open and closed loop simulations is because V_{outDC} is changed so V_x too and there is error signal at the input therefore OP parameters are changed.

$$DC \text{ diff gain} = g_{m0,1}(r_{o1} \parallel r_{o5}) * g_{m6}(r_{o6} \parallel r_{o7}),$$

$$BW \approx \frac{1}{2\pi(r_{o1} \parallel r_{o5}) * g_{m6}(r_{o6} \parallel r_{o7})C_c}, GBW = \frac{g_{m0,1}}{2\pi C_c}$$

$$PM = 90 - \tan^{-1}\left(\frac{\omega_u}{\omega_{p2}}\right), \frac{\omega_u}{\omega_{p2}} = \frac{g_{m0,1}}{C_c} * \frac{C_L}{g_{m6}}$$

Spec	closed loop simulation	hand analysis
DC gain	84.93 dB	84.93 dB
BW	363.1 Hz	472.6 Hz
GBW	6.4 MHz	6.58 MHz
PM	70.33°	75.4°

Figure 20: closed loop hand analysis

- BW, GBW & PM hand analysis are different from the simulation as the parasitic caps are large due to the large sizes and they are not taken into consideration in the hand analysis.

3. Slew rate

Figure 21: pulse settings

Test	Output	Nominal	Spec
ITI_labs:lab9_tb2:1	SR	4.501M	> 5M

Figure 22: Slew rate

We got SR less than expected due the large parasitic caps at node x so, after sweeping Cc we found that the SR & PM specs are met at $C_c = 2.3 \text{ pF}$.

Note: the results above are all with new Cc value.

Test	Output	Nominal	Spec
ITI_labs:lab9_TB2:1	SR	5.082936M	> 5M

Figure 23: Slew rate at $C_c=2.3 \text{ pF}$

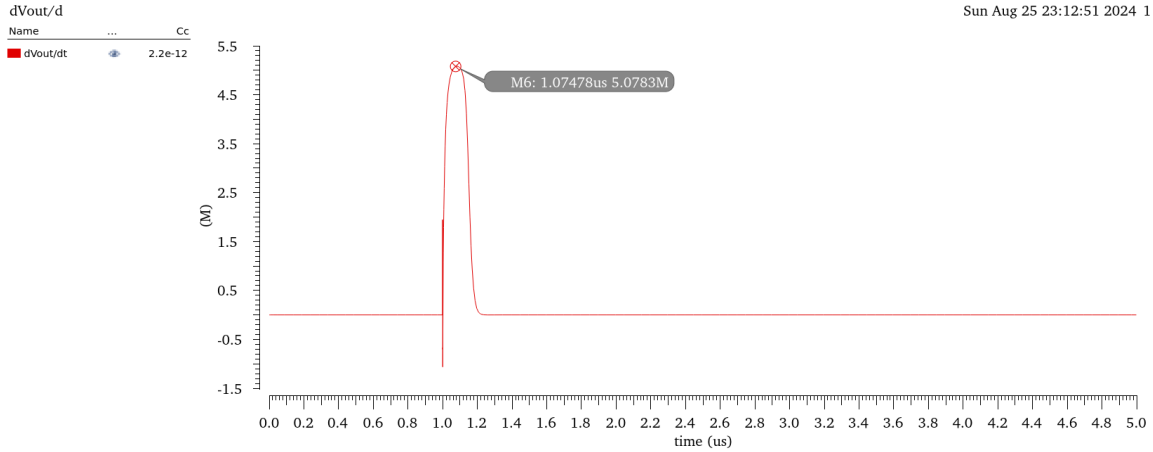


Figure 24: dVout/dt

 


Figure 25: Transient analysis Vin & Vout vs time

$$SR \approx \frac{I_{B1}}{C_c}$$

Spec	closed loop simulation	hand analysis
Slew rate	5.08 V/ μ s	5.46 V/ μ s

Table 9: simulation vs hand analysis

- The hand analysis is less than simulation result due to the parasitic caps.

4. Settling time

Property

Value

Display

Library Name

analogLib

off

Cell Name

vsources

off

View Name

symbol

off

Instance Name

V1

off

Add

Delete

Modify

User Property

Master Value

Local Value

Display

Ivignore

TRUE

off

CDF Parameter

Value

Display

DC voltage

off

Source type

pulse

off

Frequency name 1

off

Delay time

1 u s

off

Zero value

600m V

off

One value

605m V

off

Period of waveform

1 s

off

Rise time

1n s

off

Fall time

off

Type of rising & falling edge

off

Pulse width

1 s

off

Display small signal params

off

Display temperature params

off

Display noise parameters

off

Multiplier

off

OK

Cancel

Apply

Defaults

Previous

Next

Help

Figure 26: pulse settings

Test	Output	Nominal	Spec
ITI_labs:lab9_TB2:1	rise time	36.18n	< 70n

Figure 27: rise time

 


Figure 28: Vin & Vout vs time

$$T_{rise} = (\ln 9)\tau = \frac{\ln 9}{2\pi GBW}$$

<i>Spec</i>	<i>closed loop simulation</i>	<i>hand analysis</i>
<i>rise time</i>	36.18 ns	54.64 ns

- The simulation result is better as the hand analysis approximates the system to a 1st order system but in reality it's a 2nd order system which has faster response.
- There is ringing as $PM < 76^\circ$ so it's underdamped system.

Part 4: DC Closed Loop AC Open-Loop OTA Simulation

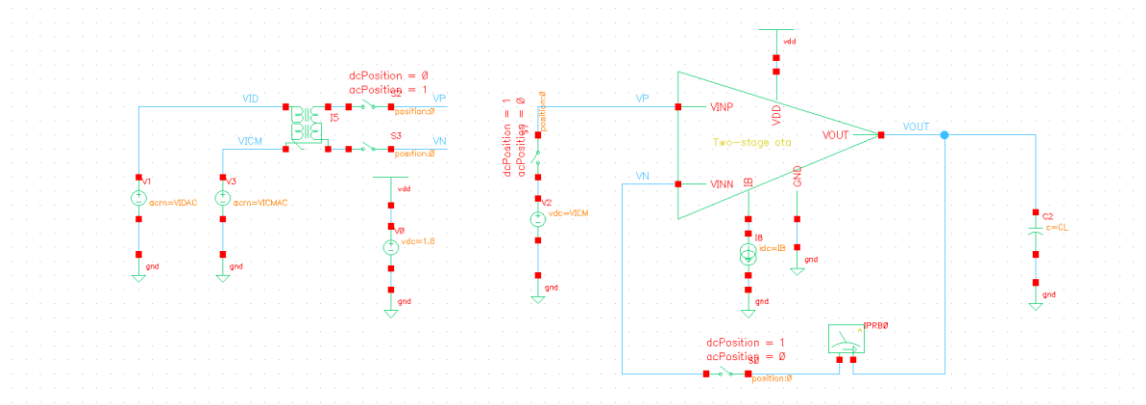


Figure 29: Testbench schematic (CL=5 pF, IB=10 uA)

1. OP simulation

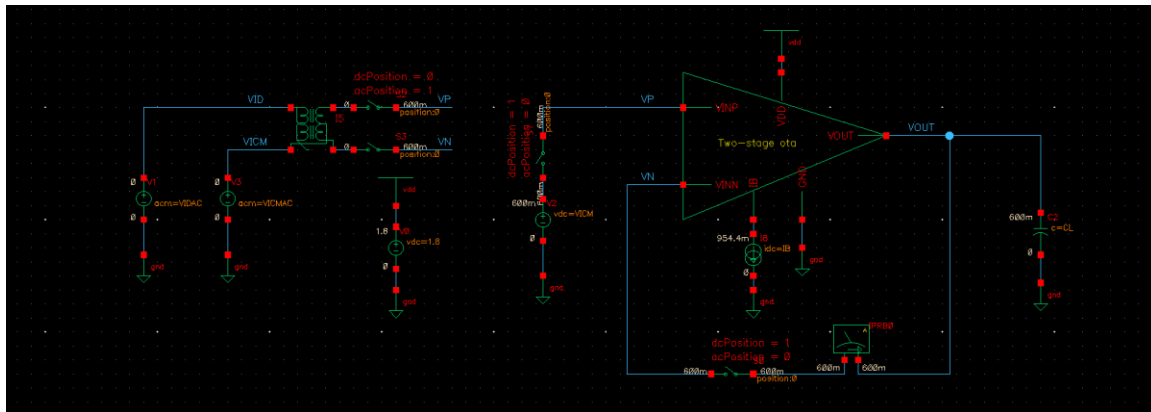


Figure 30: bias circuit with DC node voltages annotated

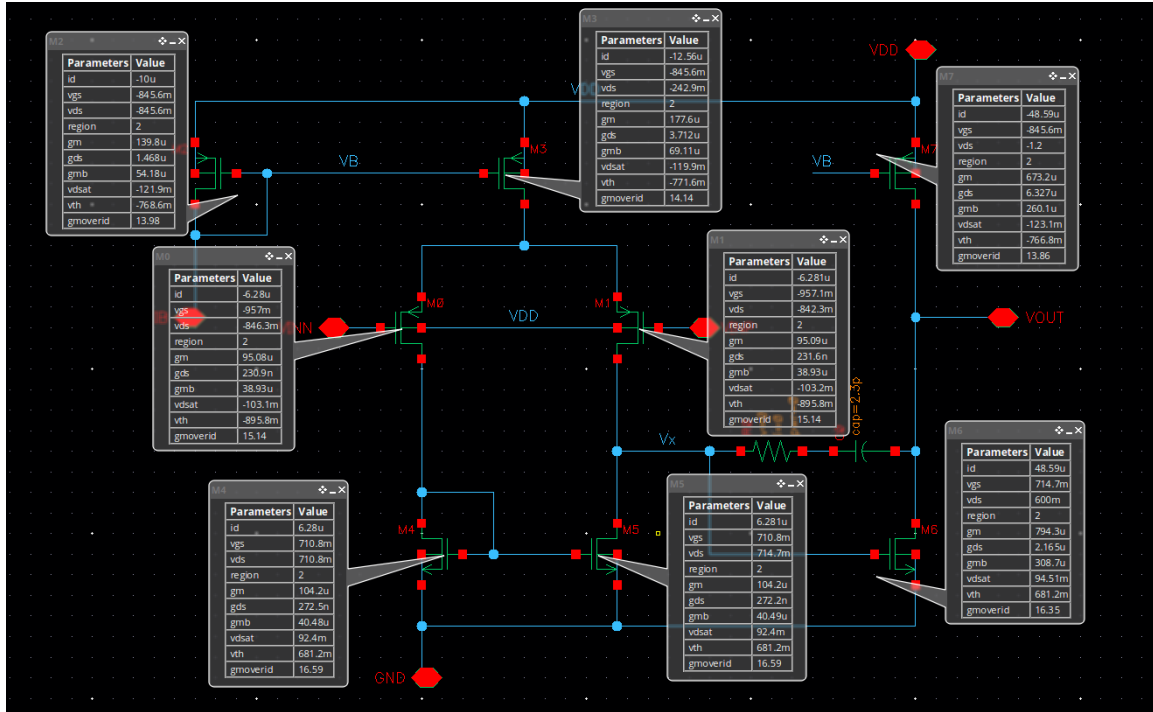


Figure 31: OTA schematic with DC node voltages and OP parameters annotated

- All devices are in sat.
- The change in g_m and I_D (about 0.02%) is due to the amplifier's very high open-loop gain which minimizes the error across its input terminals.
- The voltage difference across the OTA's terminals (differential input/error signal) is nearly zero due to the very high open-loop gain which minimizes the error signal. As the error signal equals the output deviation from its dc level divided by the amplifier's open-loop gain $= \frac{(957.6-600) \text{ mV}}{16.62 \text{ K}} \approx 21.5 \text{ } \mu\text{V}$.
- The output of the 1st stage dc level is different from its value in the open-loop simulation as the gain of the 2nd stage alone is finite and the error at this node is the output deviation from its dc level divided by the 2nd stage gain $\frac{(957.6-600) \text{ mV}}{93} \approx 3.8 \text{ mV}$.

2. Diff small signal ccs

 


Figure 32: diff gain bode plot (magnitude)

Test	Output	Nominal	Spec
ITl_labs:lab9_TB3:1	Av	17.64k	> 2k
ITl_labs:lab9_TB3:1	Av in dB	84.93	> 66
ITl_labs:lab9_TB3:1	BW	363.1	
ITl_labs:lab9_TB3:1	Fu	6.172M	> 5M
ITl_labs:lab9_TB3:1	GBW	6.421M	

Figure 33: diff small signal results

$$DC \text{ diff gain} = g_{m0,1}(r_{o1} \parallel r_{o5}) * g_{m6}(r_{o6} \parallel r_{o7}),$$

$$BW \approx \frac{1}{2\pi(r_{o1} \parallel r_{o5}) * g_{m6}(r_{o6} \parallel r_{o7})C_c}, GBW = \frac{g_{m0,1}}{2\pi C_c}$$

Spec	Simulation	Hand analysis
DC diff gain	84.93 dB	84.94 dB
BW	363.1 Hz	372.7 Hz
GBW	6.4 MHz	6.58 MHz

Table 10: simulation vs hand analysis

- BW & GBW hand analysis are different from the simulation as the parasitic caps are large due to the large sizes and they are not taken into consideration in the hand analysis.

3. CM small signal ccs

 


Figure 34: CM gain bode plot (magnitude)

Test	Output	Nominal
ITI_labs:lab9_TB3:1	Avcm	1.065
ITI_labs:lab9_TB3:1	Avcm in dB	549.8m

Figure 26: CM gain

$$DC\ CM\ gain \approx \frac{-g_{m0,1}}{2(g_{m0,1} + g_{mb0,1})g_{m4,5}r_{o3}} * g_{m6}(r_{o6} \parallel r_{o7})$$

Spec	Simulation	Hand analysis
DC CM gain	1.065	1.1

Table 11: simulation vs hand analysis

4. CMRR

 


Figure 27: CMRR bode plot (magnitude)

<i>Spec</i>	<i>Simulation</i>	<i>Hand analysis</i>
<i>CMRR</i>	84.37 dB	$A_{vd} - A_{vCM} = 84.1 \text{ dB}$

Table 12: simulation vs hand analysis

5. Diff large signal ccs

This simulation can't be done in this testbench as the diff input is OC in DC

6. CM large signal ccs (region vs VICM)

 


Figure 35: regions vs VICM

$$CMIR_{high} = V_{DD} - |V_{DSsat3}| - |V_{GS0,1}|$$

$$CMIR_{low} = -|V_{GS0,1}| + |V_{DSsat0,1}| + V_{GS4,5}$$

<i>Spec</i>	<i>simulation</i>	<i>analytic</i>
<i>CMIR_{low}</i>	—	−143 mV
<i>CMIR_{high}</i>	780 mV	693 mV

7. CM large signal ccs (GBW vs VICM)

 


Figure 36: GBW vs VICM

$$CMIR_{high} = V_{DD} - |V_{DSsat3}| - |V_{GS0,1}|$$

$$CMIR_{low} = -|V_{GS0,1}| + |V_{DSsat0,1}| + V_{GS4,5}$$

Spec	simulation	analytic
$CMIR_{low}$	105.9 mV	-143 mV
$CMIR_{high}$	784 mV	693 mV

Table 5: CMIR

The noticeable variance in the $CMIR$ is due to:

- The body effect obstacles the $CMIR_{high}$ but it also advances $CMIR_{low}$ as the VGS increases and it appears in both specs in negative.

Part 5: Design specs

<i>Spec</i>	<i>Required</i>	<i>Achieved</i>
Supply Voltage	1.8 V	1.8 V
Static gain error	$\leq 0.05 \%$	$6 * 10^{-3} \%$
CMRR @DC	$\geq 74 \text{ dB}$	83.6 dB
Phase Margin	$\geq 70^\circ$	70.33°
OTA current consumption	$\leq 60 \mu\text{A}$	58.8 μA
CMIR - high	$\geq 1 \text{ V}$	725 mV
CMIR - low	$\leq 0.2 \text{ V}$	-365 mV
Output swing	0.2 V – 1.6 V	121 mV – 1.657 V
Load	5 pF	5 pF
Buffer closed loop rise time (10% to 90%)	$\leq 70 \text{ ns}$	36.18 ns
Slew rate	5 V/ μs	5.08 V/ μs

Table 13: Design specs